

# MLSZ - WS2 : BSP 1

1.1)

$$\underline{Z}_L = j\omega L$$

$$\underline{Z}_C = \frac{1}{j\omega C}$$

$$\underline{Z}_R = R$$

$$\underline{Z}_{tot} = \underline{Z}_L + R \parallel \underline{Z}_C$$

$$= j\omega L + \frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}$$

$$= j\omega L + \frac{R}{j\omega CR + 1}$$

$$\frac{1}{\frac{1}{R} + \frac{1}{\frac{1}{j\omega C}}}$$

1.2) ZUERST  $\underline{\hat{I}}_C$  BESTIMMEN (SPANNUNGSTEILER)

$$\underline{\hat{I}}_C = \underline{\hat{I}}_0 \cdot \frac{\underline{Z}_R \parallel \underline{Z}_C}{\underline{Z}_R \parallel \underline{Z}_C + \underline{Z}_L} = \underline{\hat{I}}_0 \cdot \frac{\frac{R}{j\omega CR + 1}}{\frac{R}{j\omega CR + 1} + j\omega L} = \underline{\hat{I}}_0 \cdot \frac{R}{R + j\omega L - \omega^2 RLC}$$

ZWISCHENFRAGE : WAS IST  $\underline{\hat{I}}_R$  ?

BESTIMME  $\underline{\hat{I}}_C = \frac{\underline{\hat{I}}_C}{\underline{Z}_C} \quad (L=21)$



$$\underline{\hat{I}}_C = \frac{\underline{\hat{I}}_C}{\underline{Z}_C} = \frac{\underline{\hat{I}}_0 \cdot \frac{R}{R + j\omega L - \omega^2 RLC}}{\frac{1}{j\omega C}} = \frac{R j\omega C}{R + j\omega L - \omega^2 RLC} \cdot \underline{\hat{I}}_0$$

$$= a + b j$$

$$\downarrow$$

$$r e^{j\varphi}$$

1.3)

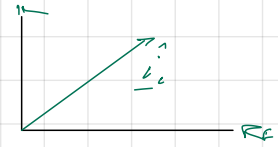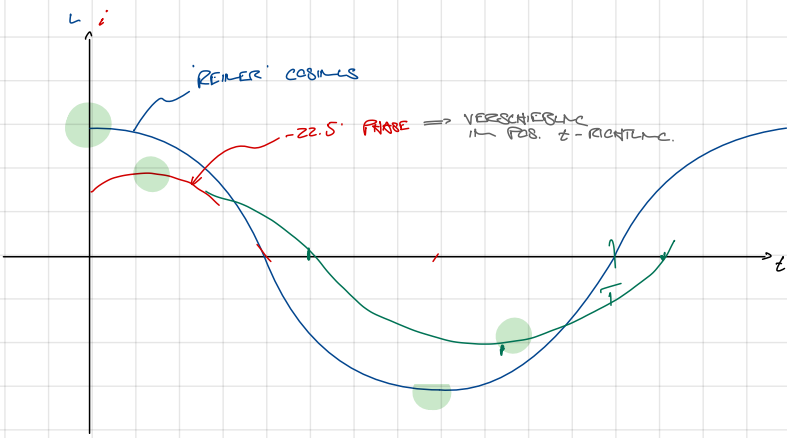


MLR QUALITATIV !:)

KONZENTRIERT WICHTIG: FREQUENZ  $\omega$  BLEIBT CONSTANT.

# BSP 1 - FEIL 2

1.4)

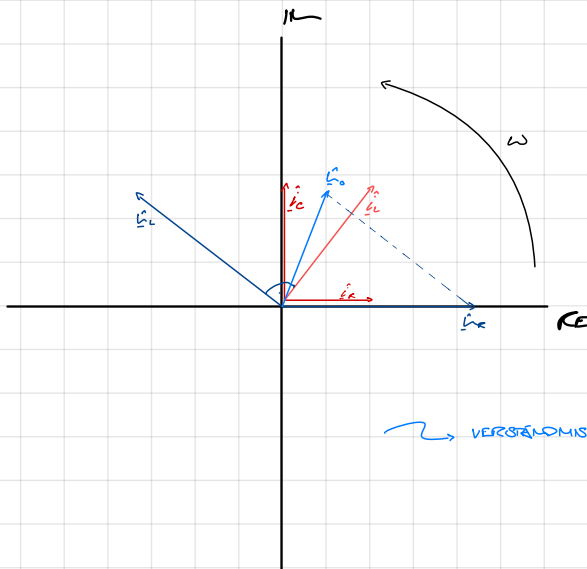

→ VERSTÄNDNISFRAGE: WO IST  $\hat{L}_c$  ?

[KURZES FR INTERLUDE]