

Bsp 1

1) RESONANZFREQUENZ : $\omega_1 = \sqrt{\frac{1}{L_1 C_1}} = \underline{\underline{10^5 \text{ Hz}}}$
 $\omega_2 = \sqrt{\frac{1}{L_2 C_2}} = \underline{\underline{10^6 \text{ Hz}}}$

↪ Q-Faktor : $Q_1 = R \sqrt{\frac{C_1}{L_1}} = \underline{\underline{10}}$
 $Q_2 = R \sqrt{\frac{C_2}{L_2}} = \underline{\underline{10}}$

2) ↪ IMPEDANZEN : $Z_1 = \frac{1}{Y_1} = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L_1} + j\omega C_1} = \frac{j\omega L_1 R}{j\omega L_1 - \omega^2 C_1 L_1 R + R}$

$$Z_2 = \left[\text{Analog} \right] = \frac{j\omega L_2 R}{j\omega L_2 - \omega^2 C_2 L_2 R + R}$$

- Gegeben $R = 1 \text{ k}\Omega$, $L_1 = 1 \text{ mH}$, $L_2 = 0.1 \text{ mH}$, $C_1 = 100 \text{ nF}$, $C_2 = 10 \text{ nF}$

$$\underline{Z_{\text{tot}}} = Z_1 \cdot Z_2 = \frac{j\omega L_1 R}{j\omega L_1 - \omega^2 C_1 L_1 R + R} \cdot \frac{j\omega L_2 R}{j\omega L_2 - \omega^2 C_2 L_2 R + R}$$

= ...

3) CHARAKTERISTISCHER TR → SICHER NICHT VOR HAND ...