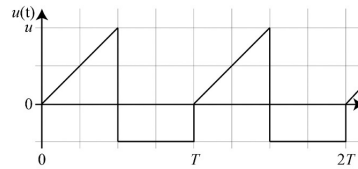



Bsp 1

Bestimmen Sie für die gezeigte Spannung

- Mittelwert \bar{u}
- Gleichrichtwert $|\bar{u}|$
- Effektivwert U
- Spitze-Spitze-Wert u_{ss}


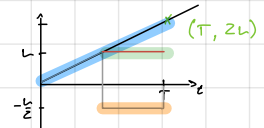
$$\begin{aligned}\text{MITTELWERT } \bar{u} &= \frac{1}{T} \int_{t_1}^{t_1+T} u(t) dt = \frac{1}{T} \int_0^T u(t) dt = \frac{1}{T} \left[\int_0^{T/2} \frac{2L}{T} t dt + \int_{T/2}^T \frac{L}{2} dt \right] \\ &= \frac{1}{T} \left[\frac{L}{T} t^2 \right]_0^{T/2} - \frac{L}{4} T \\ &= \frac{1}{T} \left[\frac{L}{4} - \frac{L}{4} \right] = 0\end{aligned}$$




$$\text{GLEICHRICHTWERT } |\bar{u}| = \frac{1}{T} \left[\int_0^{T/2} \frac{2L}{T} t dt + \int_{T/2}^T \frac{L}{2} dt \right] = \dots = \frac{L}{2}$$

$$\begin{aligned}\text{EFFEKTIVWERT } u \quad (= u_{eff}) &= \sqrt{\frac{1}{T} \int_0^T u^2(t) dt} = \sqrt{\frac{1}{T} \left[\int_0^{T/2} \frac{4L^2}{T^2} t^2 dt + \int_{T/2}^T \frac{L^2}{4} dt \right]} \\ &= \sqrt{\frac{1}{T} \left(\frac{4L^2}{3T^2} \left[\frac{t^3}{3} \right]_0^{T/2} + \frac{L^2}{4} \left[t \right]_{T/2}^T \right)} = \sqrt{\frac{1}{T} \left(\frac{4L^2 T}{24} + \frac{L^2 T}{4} - \frac{L^2 T}{8} \right)} \\ &= \sqrt{\frac{1}{T} \left(\frac{L^2 T}{6} + \frac{L^2 T}{8} \right)} = L \sqrt{\frac{7}{24}}\end{aligned}$$

$$\text{SPITZE - SPITZE - WERT } u_{ss} = \underline{\underline{\frac{3}{2} L}} \quad (\text{ABGELESEN})$$

Bsp 2

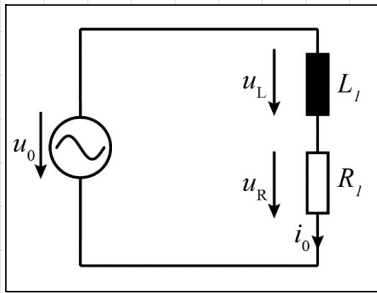


Gegeben:

$$i(t) = \hat{i} \cos(\omega t), \hat{i} = 1A, \omega = 1000Hz, R = 2\Omega, L = 1mH$$

BASIC, ABER WICHTIG: $\omega = 2\pi f = \frac{2\pi}{T}$

$$L_R(t) = R \cdot i(t) = R \cdot \hat{i} \cos(\omega t) = \underline{\underline{2 \cdot \cos(1000t)}} = 2 \cdot \sin(1000t + \frac{\pi}{2})$$
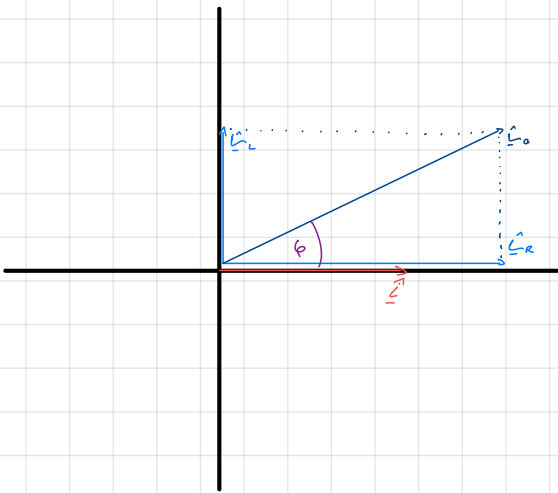
$$L_L(t) = L \cdot \frac{di(t)}{dt} = -L \cdot \underbrace{\omega}_{=1} \cdot \hat{i} \cdot \sin(\omega t) = \underline{\underline{-1 \cdot \sin(1000t)}}$$



$$L_0(0) = \underline{\underline{2V}}$$

$$i_0(0) = \hat{i} \cos(0) = \hat{i} = \underline{\underline{1A}}$$

$L(t) \hat{=}$ REALTEILE DER
ZEIGER BEI t

$$\text{AUS } \omega = 1000 \text{ Hz FOLGT DREH: } T = \frac{2\pi}{\omega} = 6.28 \cdot 10^{-3} \text{ s} \longrightarrow \frac{T}{8} = 7.85 \cdot 10^{-4} \text{ s}$$

$$\text{SONIT IST: } L_0(\frac{T}{8}) = |\underline{\underline{L_0}}| \cdot \cos(\omega \frac{T}{8} + \varphi)$$

$$= \sqrt{2^2 + 1^2} \cdot \cos(\omega \frac{T}{8} + 26.6^\circ) = \sqrt{5} \cdot \cos(\frac{11.5 \cdot \hat{i}_0}{\text{REZ} \hat{i}_0}) = \sqrt{5} \cdot \cos(\frac{1}{2}) \approx 2.6 \cdot \hat{i}$$

$\varphi = \text{PHASENVERSCHIEBUNG}$

$$= |\underline{\underline{IR}}| = \underline{\underline{0.71A}}$$

$$i(\frac{T}{8}) = \hat{i} \cos(\omega \frac{T}{8}) = |\underline{\underline{IR}}| = \underline{\underline{0.71A}}$$