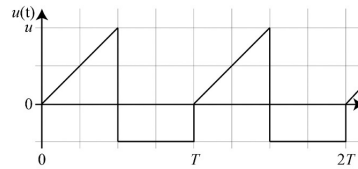



Bsp 1

Bestimmen Sie für die gezeigte Spannung

- Mittelwert \bar{u}
- Gleichrichtwert $|\bar{u}|$
- Effektivwert U
- Spitze-Spitze-Wert u_{ss}


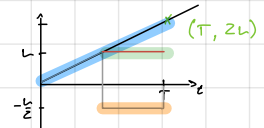
$$\begin{aligned}\text{MITTELWERT } \bar{u} &= \frac{1}{T} \int_{t_1}^{t_1+T} u(t) dt = \frac{1}{T} \int_0^T u(t) dt = \frac{1}{T} \left[\int_0^{T/2} \frac{2L}{T} t dt + \int_{T/2}^T \frac{L}{2} dt \right] \\ &= \frac{1}{T} \left[\frac{L}{T} t^2 \right]_0^{T/2} - \frac{L}{4} \left[\right] \\ &= \frac{1}{T} \left[\frac{L}{4} - \frac{L}{4} \right] = 0\end{aligned}$$




$$\text{GLEICHRICHTWERT } |\bar{u}| = \frac{1}{T} \left[\int_0^{T/2} \frac{2L}{T} t dt + \int_{T/2}^T \frac{L}{2} dt \right] = \dots = \frac{L}{2}$$

$$\begin{aligned}\text{EFFEKTIVWERT } u \quad (= u_{eff}) &= \sqrt{\frac{1}{T} \int_0^T u^2(t) dt} = \sqrt{\frac{1}{T} \left[\int_0^{T/2} \frac{4L^2}{T^2} t^2 dt + \int_{T/2}^T \frac{L^2}{4} dt \right]} \\ &= \sqrt{\frac{1}{T} \left(\frac{4L^2}{3T^2} \left[\frac{t^3}{3} \right]_0^{T/2} + \frac{L^2}{4} \left[t \right]_{T/2}^T \right)} = \sqrt{\frac{1}{T} \left(\frac{4L^2 T}{24} + \frac{L^2 T}{4} - \frac{L^2 T}{8} \right)} \\ &= \sqrt{\frac{1}{T} \left(\frac{L^2 T}{6} + \frac{L^2 T}{8} \right)} = L \sqrt{\frac{7}{24}}\end{aligned}$$

$$\text{SPITZE - SPITZE - WERT } u_{ss} = \underline{\underline{\frac{3}{2} L}} \quad (\text{ABGELESEN})$$

Bsp 2

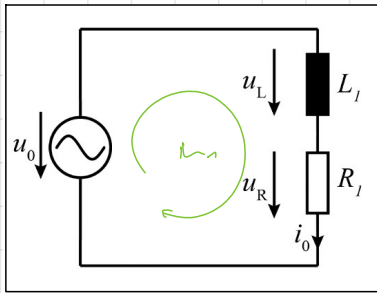

Gegeben:

$$i(t) = \hat{i} \cos(\omega t), \hat{i} = 1A, \omega = 1000Hz, R = 2\Omega, L = 1mH$$

BASIC, ABER WICHTIG: $\omega = 2\pi f = \frac{2\pi}{T}$

WIR WISSEN:

$$L_R(t) = R \cdot i(t) = R \cdot \hat{i} \cos(\omega t) = \underline{2 \cos(1000t)}$$

$$L_L(t) = L \cdot \frac{d}{dt} i(t) = \underbrace{-L \cdot \omega \cdot \hat{i}}_{=1} \sin(\omega t) = -1 \sin(1000t) = \underline{1 \cos(1000t + \frac{\pi}{2})}$$


IN BILDBEREICH:

$$\begin{aligned} \underline{\hat{i}}' &= \hat{i} \cdot e^{j\omega t} e^{j\varphi_i} \\ \underline{\hat{L}_R}' &= \hat{L}_R e^{j\omega t} e^{j\varphi_R} = R \cdot \hat{i} e^{j\omega t} e^{j\varphi_i} \\ \underline{\hat{L}_L}' &= \hat{L}_L e^{j\omega t} e^{j\varphi_L} = L \omega \hat{i} e^{j\omega t} e^{j\varphi_i} \end{aligned}$$

$\varphi_i = 0$, DA ES SICH UM EINEN BEZUGS WERT HANDELT.
 $\varphi_R = 0$, "
 $\varphi_L = +\frac{\pi}{2}$

$$@ t=0 : i(t=0) = \text{Re}\{\underline{\hat{i}}'\} = \text{Re}\{\hat{i} \cdot e^{j\omega t} e^{j\varphi_i}\} = \hat{i} \cdot \cos(\varphi_i) = \hat{i} \cdot \cos(0) = \hat{i} = \underline{1A}$$
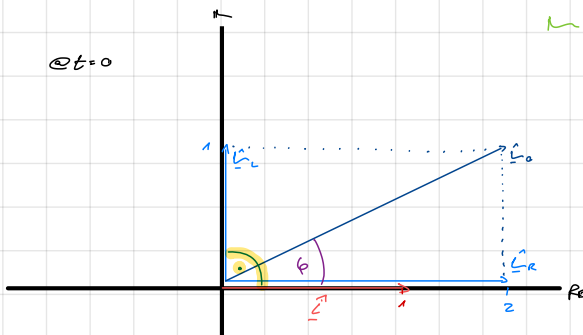
$$L_R(t=0) = \text{Re}\{\underline{\hat{L}_R}'\} = \text{Re}\{\hat{L}_R e^{j\omega t} e^{j\varphi_R}\} = R \hat{i} \cos(\varphi_R) = R \hat{i} = \underline{2V}$$



MAN: $\underline{\hat{L}}_0' = \underline{\hat{L}}_R' + \underline{\hat{L}}_L'$ Vlt, ABER NUR FÜR $t=0 \dots [V]$

($\varphi_R=0$)

$$\begin{aligned} \underline{\hat{L}}_0 &= R \cdot \hat{i} e^{j\omega t} + L \omega \hat{i} e^{j\omega t} e^{j\frac{\pi}{2}} \\ &= 2 + j1 = a + jb \\ &= \sqrt{5} e^{j26.6^\circ} = r e^{j\varphi} \end{aligned}$$

ALS $\omega = 1000 \text{ Hz}$ FOLGT DREH: $T = \frac{2\pi}{\omega} = 6.28 \cdot 10^{-3} \text{ s} \implies \frac{T}{8} = 7.85 \cdot 10^{-4} \text{ s}$

SOMIT IST: $L_0(T/8) = |\underline{\hat{L}}_0| \cdot \cos(\omega \frac{T}{8} + \varphi)$

φ = PHASEVERSCHIEBUNG

$= \arctan\left(\frac{1.5 \underline{\hat{L}}_0'}{\text{Re}\{\underline{\hat{L}}_0'\}}\right) = \arctan\left(\frac{1}{2}\right) \approx 26.6^\circ$

DIESE PHASEVERSCHIEBUNG φ BLEIBT KONSTANT.

$$= \sqrt{2^2 + 1^2} \cdot \cos(\omega \frac{T}{8} + 26.6^\circ)$$

$$= |\underline{TR}| = \underline{0.71A}$$

$$i(\frac{T}{8}) = \hat{i} \cos(\omega \frac{T}{8}) = |\underline{TR}| = \underline{0.71A}$$