
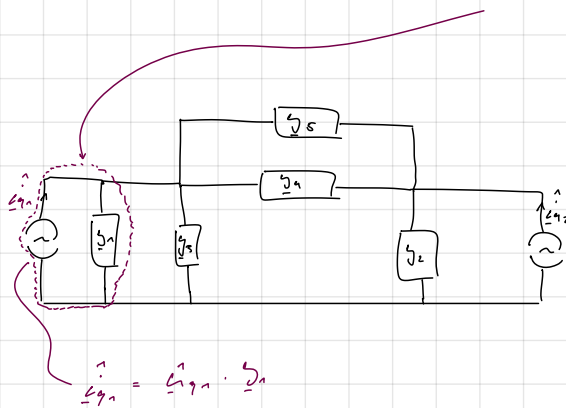


# MLSZ - W08 : Bsp 1

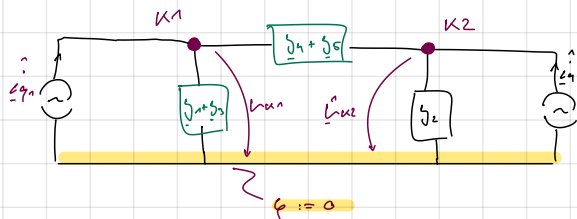a) (ENTWEDER SUPERKnoten) ODER REIZE SPANNUNGSQUELLE UMWANDeln (IN STROMQUELLE)



b)  
c) d)



$$\begin{aligned} \Rightarrow \quad K1: \quad & (\underline{y}_3 + \underline{y}_1) [\underline{\hat{L}}_{K1}] + (\underline{y}_1 + \underline{y}_5) [\underline{\hat{L}}_{K1} - \underline{\hat{L}}_{K2}] - \underline{\hat{L}}_{q1} = 0 \\ K2: \quad & \underline{y}_2 [\underline{\hat{L}}_{K2}] + (\underline{y}_1 + \underline{y}_5) [\underline{\hat{L}}_{K2} - \underline{\hat{L}}_{K1}] - \underline{\hat{L}}_{q2} = 0 \end{aligned}$$

$$\begin{aligned} \Leftrightarrow \quad K1: \quad & \underline{\hat{L}}_{K1} (\underline{y}_1 + \underline{y}_3 + \underline{y}_1 + \underline{y}_5) + \underline{\hat{L}}_{K2} (-\underline{y}_1 - \underline{y}_5) = \underline{\hat{L}}_{q1} \\ K2: \quad & \underline{\hat{L}}_{K1} (-\underline{y}_1 - \underline{y}_5) + \underline{\hat{L}}_{K2} (\underline{y}_2 + \underline{y}_1 + \underline{y}_5) = \underline{\hat{L}}_{q2} \end{aligned}$$


$$\Leftrightarrow \begin{bmatrix} (\underline{y}_1 + \underline{y}_3 + \underline{y}_1 + \underline{y}_5) & (-\underline{y}_1 - \underline{y}_5) \\ (-\underline{y}_1 - \underline{y}_5) & (\underline{y}_2 + \underline{y}_1 + \underline{y}_5) \end{bmatrix} \begin{bmatrix} \underline{\hat{L}}_{K1} \\ \underline{\hat{L}}_{K2} \end{bmatrix} = \begin{bmatrix} \underline{\hat{L}}_{q1} \\ \underline{\hat{L}}_{q2} \end{bmatrix}$$

$$\begin{aligned} \Rightarrow \quad \text{TR :)} \quad & \rightarrow \underline{\hat{L}}_{K1} = \underline{\quad} \\ & \underline{\hat{L}}_{K2} = \underline{\quad} \end{aligned}$$

$$\Rightarrow \underline{\hat{L}}_2 = \underline{\hat{L}}_{K2} \cdot \underline{y}_2 = \underline{\quad}$$

# MLSZ - W08 :    ÜSP 2

a)

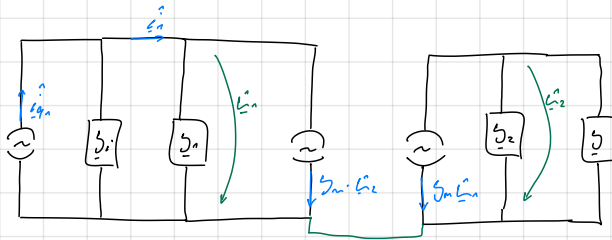


$$y_i = \frac{1}{z_i}$$

$$i_{g1} = \frac{u_{g1}}{z_i}$$

$$y = \frac{1}{z}$$

b)

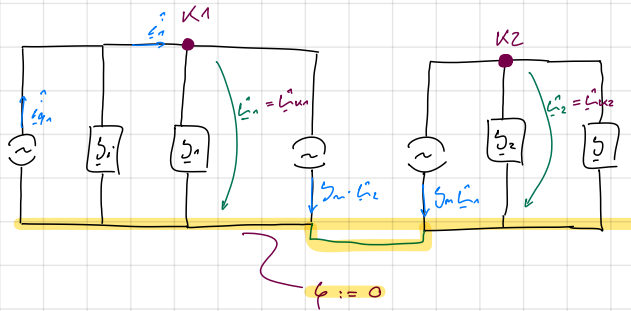

$$\rightarrow \text{K1: } -i_{g1} + (y_i + y_n) i_{u1} + y_m i_{u2} = 0$$

$$\text{K2: } y_m i_{u1} + (y_2 + y) i_{u2} = 0$$

$$\Leftrightarrow \begin{bmatrix} (y_i + y_n) & y_m \\ y_m & (y_2 + y) \end{bmatrix} \begin{bmatrix} i_{u1} \\ i_{u2} \end{bmatrix} = \begin{bmatrix} i_{g1} \\ 0 \end{bmatrix}$$

$$\Rightarrow \text{VR : )}$$

$$\rightarrow i_{g2} = i_{u2} \cdot y \quad \rightarrow \dots = \frac{y}{(y_i + y_n)(y_2 + y) - y_m^2} \cdot (-y_m) \cdot i_{g1} = i_{g2}$$